

## PROJECT REPORT

### UNIVERSAL SYNCHRONOUS DECADE COUNTER

#### OBJECTIVE: -

To make a universal synchronous counter using Flip Flops.

#### ABSTRACT: -

The ICs used as counters are available in market, but if want to make a counter of mode 100 using two synchronous counters of mode 10 connected in cascade, it will not work because we have to apply clock pulse at same instant to both counters. Hence it will be a failure.

Our aim is to make a universal synchronous counter connected in cascade, for example we have two synchronous counters connected in cascade it will be counter of mode 100. And if we connect it with another synchronous counter it will be a mode 1000 counter which is a good thing.

#### APPARATUS: -

- AND gate (7408)
- J-K Flip-Flops (IC7473)
- LEDs
- 7-Segment Display
- BCD to 7-segment decoder (74LS47)
- MUX (74151)
- Resistors
- Buttons
- Jumper wires

 


Figure 1: 7408 AND gate

 


Figure 2: 7473 jk Flip-Flop

 


Figure 3: Common anode 7 Segment

 


Figure 4: 7447 BCD Decoder

 


Figure 5: 74151 Multiplexer

### **LOGIC: -**

The aim is that we have to make a synchronous decade counter using flip flops and combinational circuits. Master slave negative edge triggered j-k flip flops are used, we are using j-k flip flops due to the toggling ability of j-k flip flops. We can use them as T-flip flops by short circuiting the j and k inputs.

Now we have added a pin named "M" it mean mode if the pin "M" is 0 it will count up and if pin is HIGH or 1 it will count down. And the state diagram of the BCD up down counter is simple as shown below: -

 


Figure 6: State diagram of BCD up counter

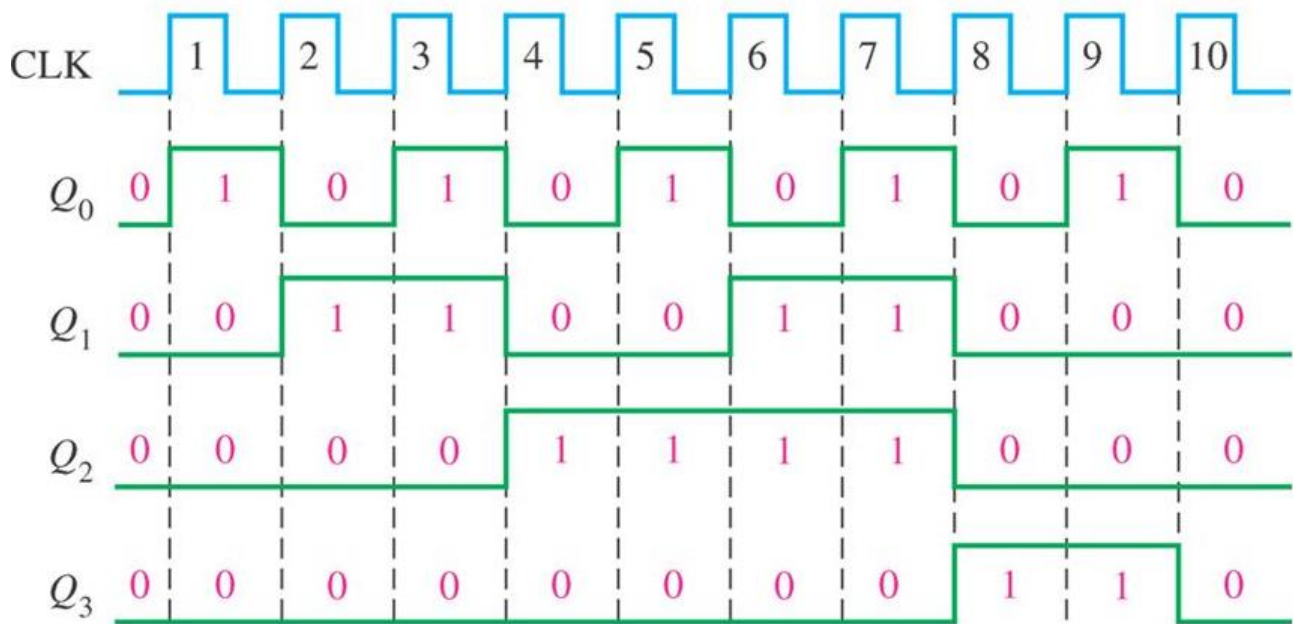


Figure 7: Timing Diagram of BCD up counter

The above diagram is a timing diagram for a decade up counter. Here, when a clock pulse is changing from low to high, it counts the clock pulse and shows the output in binary form. Every clock pulse is given to the other J-K flip-flop, which will change its state when the previous one changes the state.

It can be called a universal counter because when we cascade two counters using an OR gate, then there will be such conditions that when the previous counter approaches 9 and after that to 0, then the next one counts to 1 and so on to 2. Thus, it can count to 99 in a synchronous manner. By cascading two counters, we can make a 100-mode counter, and cascading of three counters will give a counter of mode 1000 and will count from 0 to 999.

Truth table used for the logic is shown below: -

Selection	Previous States				Next States				Flip Flop Inputs			
M	Q4	Q3	Q2	Q1	Q4*	Q3*	Q2*	Q1*	T4	T3	T2	T1
0	0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	1	0	0	1	0	0	0	1	1
0	0	0	1	0	0	0	1	1	0	0	0	1
0	0	0	1	1	0	1	0	0	0	1	1	1
0	0	1	0	0	0	1	0	1	0	0	0	1
0	0	1	0	1	0	1	1	0	0	0	1	1
0	0	1	1	0	0	1	1	1	0	0	0	1
0	0	1	1	1	1	0	0	0	1	1	1	1
0	1	0	0	0	1	0	0	1	0	0	0	1
0	1	0	0	1	0	0	0	0	1	0	0	1
0	1	0	1	0	x	x	x	x	x	x	x	x
0	1	0	1	1	x	x	x	x	x	x	x	x
0	1	1	0	0	x	x	x	x	x	x	x	x
0	1	1	0	1	x	x	x	x	x	x	x	x
0	1	1	1	0	x	x	x	x	x	x	x	x
0	1	1	1	1	x	x	x	x	x	x	x	x
1	0	0	0	0	1	0	0	1	1	0	0	1
1	0	0	0	1	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	1	0	0	1	1
1	0	0	1	1	0	0	1	0	0	0	0	1
1	0	1	0	0	0	0	1	1	0	1	1	1
1	0	1	0	1	0	1	0	0	0	0	0	1
1	0	1	1	0	0	1	0	1	0	0	1	1
1	0	1	1	1	0	1	1	0	0	0	0	1
1	1	0	0	0	0	1	1	1	1	1	1	1
1	1	0	0	1	1	0	0	0	0	0	0	1
1	1	0	1	0	x	x	x	x	x	x	x	x
1	1	0	1	1	x	x	x	x	x	x	x	x
1	1	1	0	0	x	x	x	x	x	x	x	x
1	1	1	0	1	x	x	x	x	x	x	x	x
1	1	1	1	0	x	x	x	x	x	x	x	x
1	1	1	1	1	x	x	x	x	x	x	x	x
1	1	1	1	1	x	x	x	x	x	x	x	x

Here Q4, Q3, Q2 and Q1 are previous states of flip flops, M is selection pin for mode selection, Q4\*, Q3\*, Q2\*, Q1\* are next states of the flip flop based on the inputs T4, T3, T2 and T1.

Don't care "X" are used for 4-bit numbers not included in BCD and the outputs not required in circuit.

By reduction method we found the following expressions for the counter circuit,

$$T_4 = \overline{M}Q_4Q_1 + \overline{M}Q_3Q_2Q_1 + M\overline{Q_3}\overline{Q_2}\overline{Q_1}$$

$$T_3 = \overline{M}Q_2Q_1 + MQ_3\overline{Q_2}\overline{Q_1} + MQ_D\overline{Q_2}\overline{Q_1}$$

$$T_2 = M\overline{Q_4}Q_1 + MQ_3\overline{Q_1} + MQ_D\overline{Q_1}$$

$$T_1 = \overline{M}\overline{Q_4}Q_1 + MQ_2\overline{Q_1} + MQ_3\overline{Q_1} + MQ_D\overline{Q_1}$$

### CIRCUIT: -

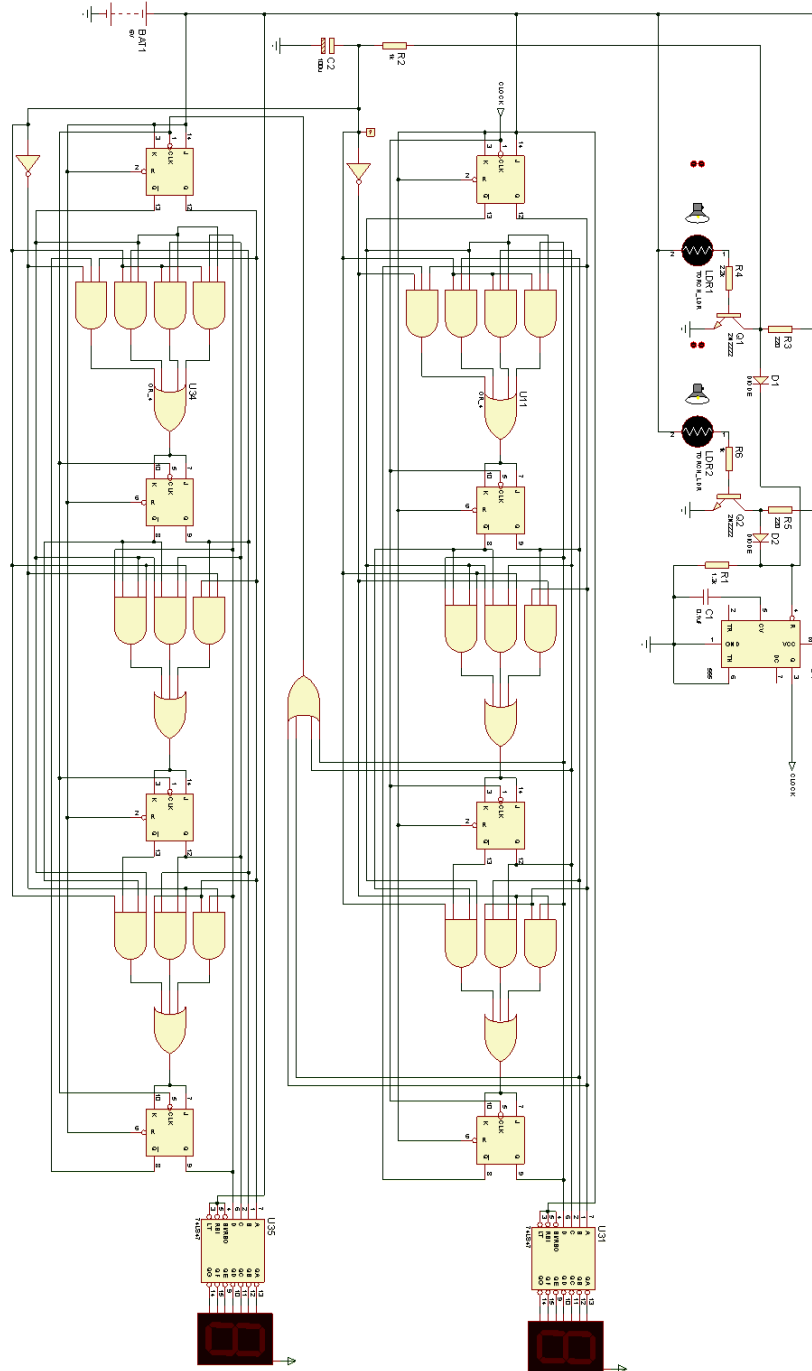


Figure 8: Circuit without reduction of mode 100 counter

The circuit was massive and huge so we considered to use MUX for implementation of combinational logics between two consecutive flip flops. Then we have a circuit using 8 x 1 MUX which is reduced to about half of the size.

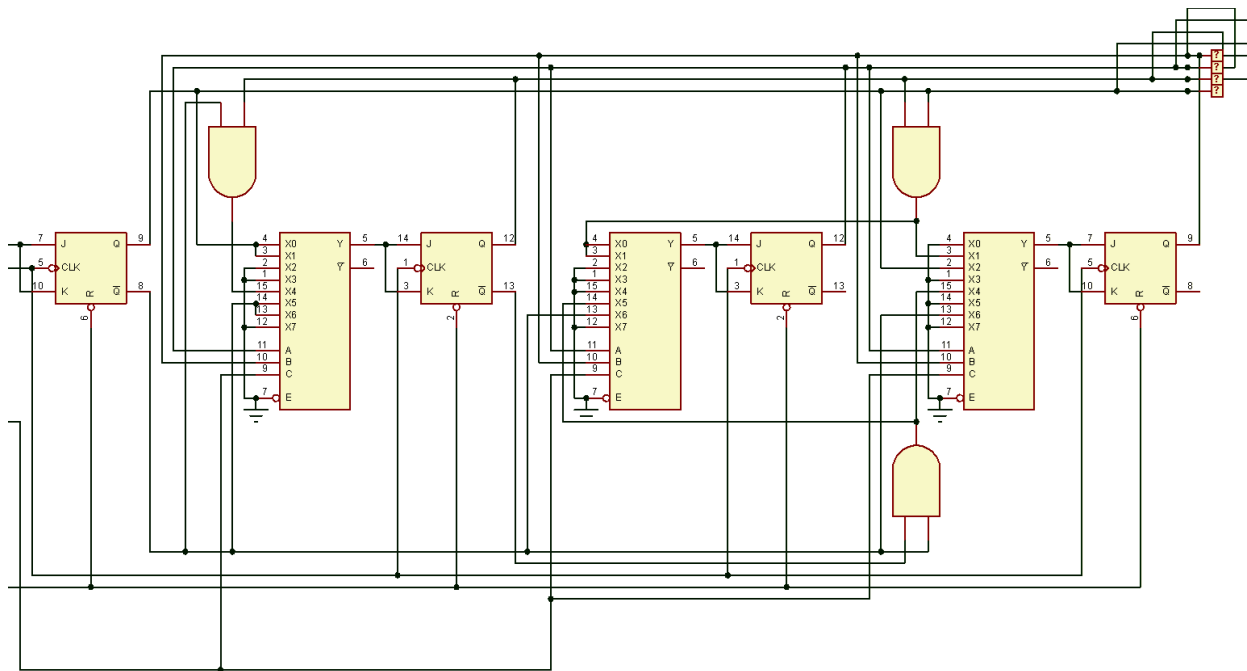


Figure 9: Circuit of mode 10 counter after reduction

We have implemented the combinational parts of the circuit using only 3 AND gates and MUX by reduction methods otherwise we have to use 64 AND gates for a flip flop which will be a massive and huge circuit.

### **CONCLUSION: -**

The conclusion of the project is that we have implemented a circuit that can be used as a universal synchronous counter by cascading method of our desired mode.

- We can convert mode 10 counter to mode 100 counter by cascading two counters and an OR gate between them.
- We have reduced the circuit from a huge size to a small size by using MUX.
- A fast synchronous universal counter has been implemented.

### **SUBMITTED BY: -**

- 2019 MC 255
- 2019 MC 263
- 2019 MC 273
- 2019 MC 281